

Q1  
a)

Decimal	Binary	Hexadecimal
546	$(10001\ 00010)_2$	$(222)_{16}$
128	$(1000\ 0000)_2$	$(80)_{16}$
27.375	$(11011.011)_2$	$(1B.6)_{16}$

23.395:

$$\begin{aligned}
 0.375 \times 2 &= 0.75 \rightarrow 0 \\
 0.75 \times 2 &= 1.5 \rightarrow 1 \\
 0.5 \times 2 &= 1.0 \rightarrow 1
 \end{aligned}$$

in binary =

11011.011

$$\begin{array}{r}
 546 \quad | \quad 2 \\
 -293 \quad | \quad 2 \\
 \hline
 0 \quad = \quad 136 \quad | \quad 2 \\
 \quad | \quad = \quad 0 \quad = \quad 68 \quad | \quad 2 \\
 \quad \quad | \quad = \quad 0 \quad = \quad 34 \quad | \quad 2 \\
 \quad \quad \quad | \quad = \quad 0 \quad = \quad 17 \quad | \quad 2 \\
 \quad \quad \quad \quad | \quad = \quad 0 \quad = \quad 8 \quad | \quad 2 \\
 \quad \quad \quad \quad \quad | \quad = \quad 1 \quad = \quad 4 \quad | \quad 2 \\
 \quad \quad \quad \quad \quad \quad | \quad = \quad 0 \quad = \quad 2 \quad | \quad 2 \\
 \quad \quad \quad \quad \quad \quad \quad | \quad = \quad 0 \quad = \quad 0 \quad | \quad 1 \\
 \quad \quad \quad \quad \quad \quad \quad \quad | \quad = \quad 0 \quad = \quad 0 \quad | \quad 0
 \end{array}$$

$128 = 2^7 = (1000\ 0000)_2$   
 $1000\ 0000$   
 $\quad \downarrow \quad \downarrow$   
 $\quad 8 \quad 0$

Decimal	Signed 8-bit binary in 2's complement form
-6.375	$(1111\ 1001.101)_2$

6.375 in signed 8-bit binary in 2's complement

frm: 0000 0110.011

↓ 1's complement

$$\begin{array}{r}
 1111\ 1001.100 \\
 + \quad \quad \quad 1 \\
 \hline
 1111\ 1001.101
 \end{array}
 \quad = -\cancel{25} -\cancel{16} -\cancel{8} -7 \\
 = -7 + 0.625 = \underline{\underline{-6.375}}$$

Signed 8-bit binary in 2's complement form	Decimal
00000011.1101	$(3.8125)_{10}$
11111111.1111	$(-0.0625)_{10}$
10100110.0111	$(-89.5625)_{10}$

$$\begin{array}{r} 0000 \quad 0011.1101 \\ \hline 3 \quad + \quad 0.5 + 0.25 + 0.0625 = 0.8125 = 3.8125 \end{array}$$

$$\begin{aligned}
 1111111.1111 &= -128 + 64 + 32 + 16 + 8 + 4 + 2 + 1 + 0.5 + 0.25 + 0.125 + 0.0625 \\
 &= -1 + 0.5 + 0.25 + 0.125 + 0.0625 \\
 &= -0.0625
 \end{aligned}$$

$$\begin{aligned}
 10100110.0111 &= -128 + 64 + 32 + 16 + 8 + 4 + 2 + 1 + 0.25 + 0.125 + 0.0625 \\
 &= -90 + \underbrace{0.25 + 0.125 + 0.0625}_{\text{error}} \\
 &= -90 + 0.4375 = -89.5625
 \end{aligned}$$

- b) (10 pt) Calculate the binary equivalent of  $127/64$ . If we use only 4 bits in the fraction, what is the error in the binary representation? How many bits are needed to fully represent  $127/64$  in signed 2's complement binary number system? Show your work clearly.

$$\frac{127}{64} = \frac{2^6 + 2^5 + 2^4 + 2^3 + 2^2 + 2^1 + 2^0}{2^6} = 2^0 + 2^{-1} + 2^{-2} + 2^{-3} + 2^{-4} + 2^{-5} + 2^{-6}$$

$$2^0 + 2^{-1} + 2^{-2} + 2^{-3} + 2^{-4} + 2^{-5} + 2^{-6} = \underbrace{(1.1111)_2}_{=(1.984375)_{10}} = 1 + 0.5 + 0.25 + 0.125 + 0.0625 + 0.03125 + 0.015625$$

$$\begin{aligned}
 \text{if we only use 4 bits in the fraction} &= \text{the number becomes} = (1.111)_2 = 1 + 0.5 + 0.25 + 0.125 + 0.0625 \\
 &= 1.9375
 \end{aligned}$$

an error in binary fraction occurs. The difference between the numbers =  $1.98 - 1.9375$   
 $= \underline{0.046875}$

how many bits needed to fully represent  $27/64$  in signed 2's complement binary number system?

2 bits needed for number part, as it is 01 and for fraction part 6 bits needed to fully represent the fraction part. So in total 2 for number + 6 for fraction = 8 bits needed

Q2)

Assume a 5-bit, 2's complement scheme to represent signed integers.

a) (3 pt) Show the range of integers that can be represented.

Range is between  $[(10000)_2, (01111)_2]$ , in decimal it is equivalent to  $[-16]_{10}, [15]_{10}$

b) (12 pt) Do the following arithmetic operations and detect overflows. Show your work clearly.

$14 + 9$  overflow

$14 + (-9)$  no overflow

$(-5) + (-9)$  no overflow

$(-7) + (-10)$  overflow

$$\begin{array}{r} 14 = 01110 \\ + 9 = 01001 \\ \hline \cancel{X}101\ 11 = -(6+4+2+1) \\ = -9 \quad X \\ \text{overflow!} \end{array}$$

$$\begin{array}{r} 14 = 01110 \\ 9 = 01001 \rightarrow -9 = 10111 \\ \begin{array}{r} 111 \\ 01110 \\ + 10111 \\ \hline \cancel{X}00101 = 4+1=5 \quad \checkmark \end{array} \end{array}$$

$$\begin{array}{r} 5 = 00101 \quad 9 = 01001 \\ -5 = 11011 \quad -9 = 10111 \\ \begin{array}{r} 11111 \\ 11011 \\ + 10111 \\ \hline \cancel{X}10010 = -16+2=-14 \quad \checkmark \end{array} \end{array}$$

$$\begin{array}{r} 7 = 00111 \rightarrow -7 = 11001 \\ 10 = 01010 \rightarrow -10 = 10110 \\ \begin{array}{r} 11001 \\ + 10110 \\ \hline \cancel{X}01111 = 8+4+2+1=15 \quad X \end{array} \end{array}$$

Q3)


a) (5 pt) Express the following function as a sum of minterms.

$$F(x,y,z,t) = (x \oplus y)(z+t)$$

	x	y	z	t	$x \oplus y$	$z+t$	$F(x,y,z,t)$
$m_0$	0	0	0	0	0	0	0
$m_1$	0	0	0	1	0	1	0
$m_2$	0	0	1	0	0	1	0
$m_3$	0	0	1	1	0	1	0
$m_4$	0	1	0	0	1	0	0
$m_5$	0	1	0	1	1	1	1
$m_6$	0	1	1	0	1	1	1
$m_7$	0	1	1	1	1	1	1
$m_8$	1	0	0	0	1	0	0
$m_9$	1	0	0	1	1	1	1
$m_{10}$	1	0	1	0	1	1	1
$m_{11}$	1	0	1	1	1	1	1
$m_{12}$	1	1	0	0	0	0	0
$m_{13}$	1	1	0	1	0	1	0
$m_{14}$	1	1	1	0	0	1	0
$m_{15}$	1	1	1	1	0	1	0


$$\begin{aligned}
 F(x,y,z,t) &= m_5 + m_6 + m_7 + m_9 + m_{10} + m_{11} \\
 &= \sum(5, 6, 7, 9, 10, 11) \\
 &= x'y'z't + x'yzt' + x'yzt + xy'z't + \\
 &\quad xy'zt' + xy'zt
 \end{aligned}$$

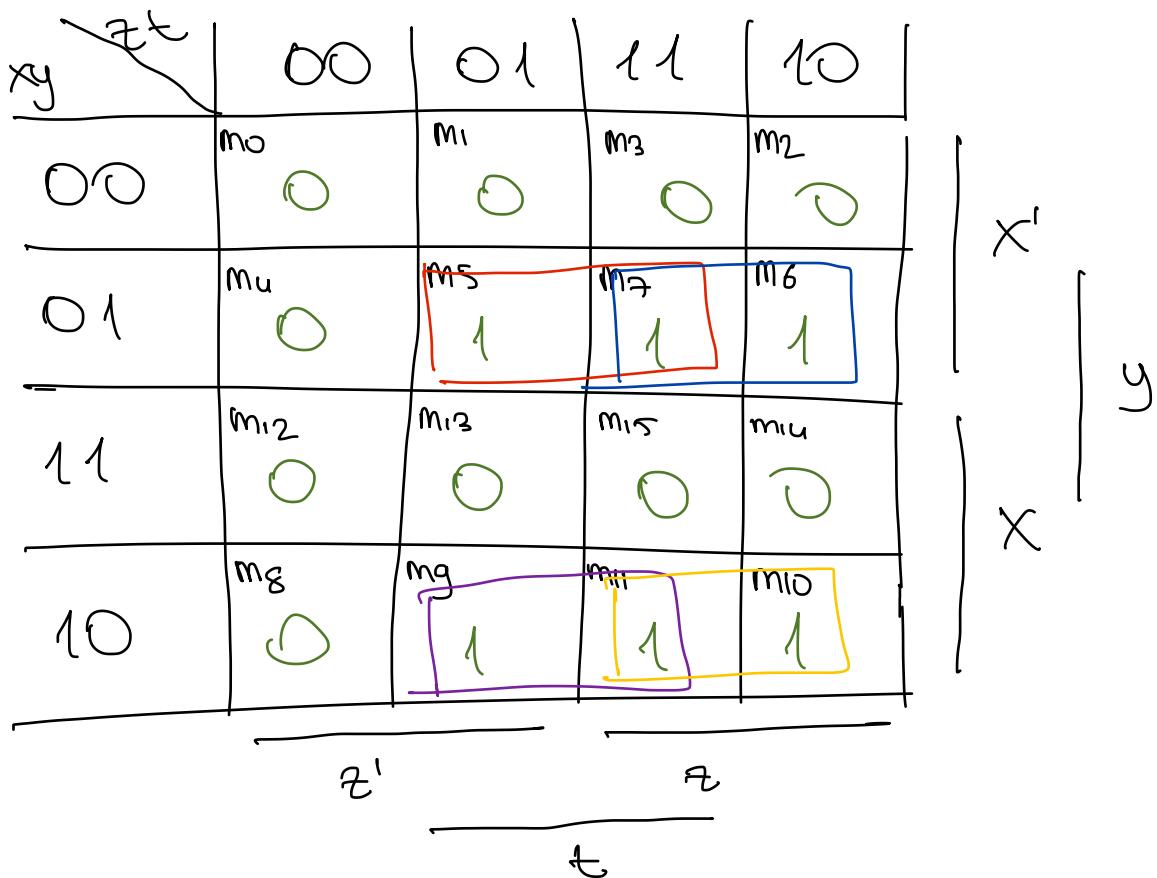b) (10 pt) Optimize F using Karnaugh map.



$$F(x,y,z,t) = x'yzt + x'yz + xy't + xy'z$$

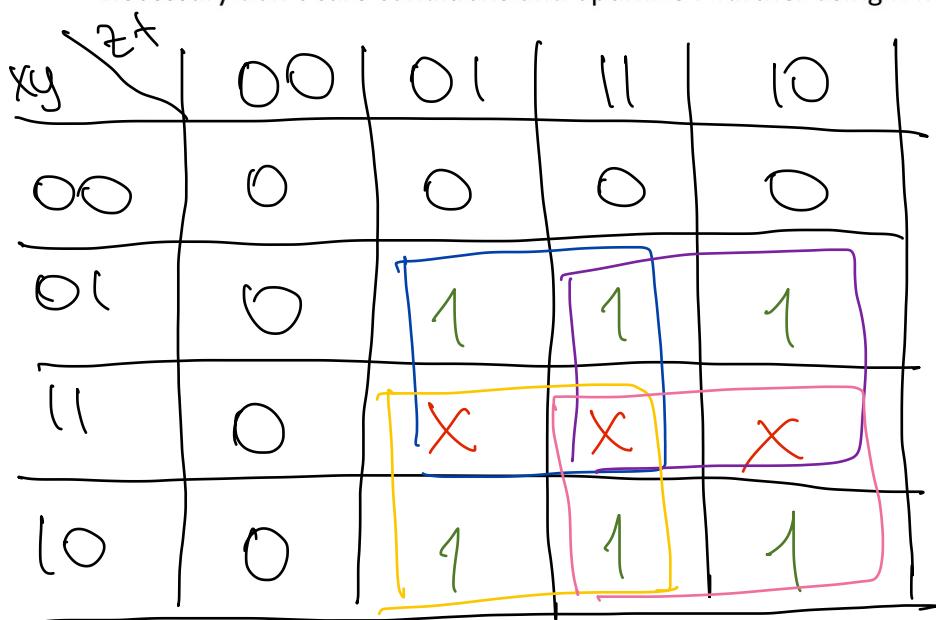c) (5 pt) Assume we guarantee that  $xyzt_2$  will never be larger than 12. Add necessary don't care conditions and optimize F further using K-map.




$$F(x,y,z,t) = yt + yz + xt + xz$$

can further optimize with ad-hoc:

$$= y(t+z) + x(t+z) = (t+z)(x+y)$$

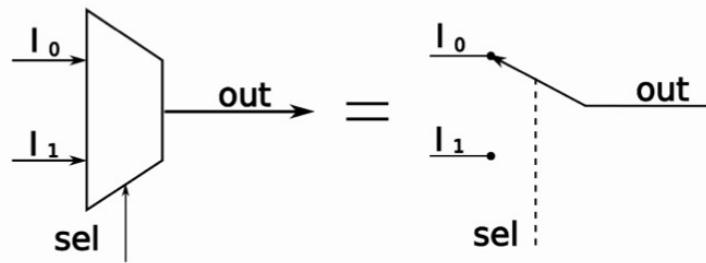**Q4**) Multiplexer is a logical unit that selects between several input signals.




For a 2-to-1 multiplexer, if the sel input is 0, out output is equal to  $I_0$ . If the sel input is 1, out output is equal to  $I_1$ . Design this 2-to-1 multiplexer and draw its circuit.

$$\text{Multiplexer} = I_0 \cdot \text{sel}' + I_1 \cdot \text{sel}$$

$$\text{if } \text{sel} = 0 \rightarrow \text{sel}' = 1 \rightarrow \text{Multiplexer} = I_0$$
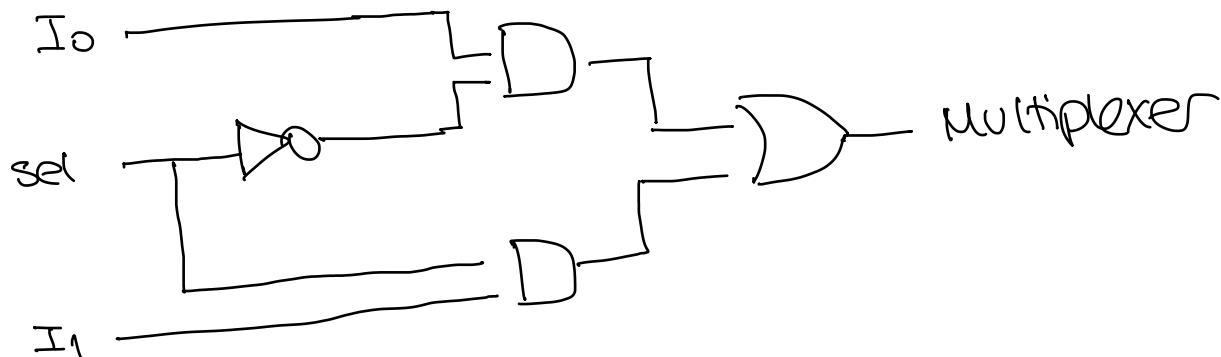
$$\text{if } \text{sel} = 1 \rightarrow \text{sel}' = 0 \rightarrow \text{Multiplexer} = I_1$$



**Q5**) You are asked to design a 2-bit comparator circuit. Operation of this circuit is defined as follows:

**Inputs:**  $A = (A_1, A_0)_2$  and  $B = (B_1, B_0)_2$ , 2-bit signed numbers in 2's complement form

**Outputs:** EQ, G, L

if ( $A == B$ ) EQ=1 else EQ=0	if ( $A < B$ ) L=1 else L=0	if ( $A > B$ ) G=1 else G=0
---	--------------------------------------	--------------------------------------

Design circuit for this comparator, however you would like to design it and draw its circuit. You can use deductions as we used in class. For example, if you have a circuit for EQ output, and a circuit for L output, you can use those two outputs to derive G output. Show your work clearly.

Truth Table:

	$A_1$	$A_0$	$B_1$	$B_0$	$EQ$	$L$	$G$
$m_0$	0	0	0	0	1	0	0
$m_1$	0	0	0	1	0	1	0
$m_2$	0	0	1	0	0	0	1
$m_3$	0	0	1	1	0	0	1
$m_4$	0	1	0	0	0	0	1
$m_5$	0	1	0	1	1	0	0
$m_6$	0	1	1	0	0	0	1
$m_7$	0	1	1	1	0	0	1
$m_8$	1	0	0	0	0	1	0
$m_9$	1	0	0	1	0	1	0
$m_{10}$	1	0	1	0	1	0	0
$m_{11}$	1	0	1	1	0	1	0
$m_{12}$	1	1	0	0	0	1	0
$m_{13}$	1	1	0	1	0	1	0
$m_{14}$	1	1	1	0	0	0	1
$m_{15}$	1	1	1	1	1	0	0

$$EQ = \sum(0, 5, 10, 15)$$

$$L = \sum(1, 8, 9, 11, 12, 13)$$

$$G = \sum(2, 3, 4, 6, 7, 14)$$

$$G = EQ' \cdot L' = (EQ + L)'$$

Karnaugh-map for  $EQ$ :

	$B_1B_0$	00	01	11	10
$A_1A_0$	00	1	0	0	0
00	00	1	0	0	0
01	00	0	1	0	0
11	00	0	0	1	0
10	00	0	0	0	1

$$EQ = A_1'A_0'B_1'B_0' + A_1'A_0B_1'B_0 + A_1A_0B_1B_0 + A_1A_0'B_1B_0'$$

$$= A_1'B_1'(A_0'B_0' + A_0B_0) + A_1B_1(A_0B_0 + A_0'B_0')$$

$$= \underbrace{(A_0B_0 + A_0'B_0')}_{XNOR} \underbrace{(A_1B_1 + A_1'B_1')}_{XNOR}$$

$$= (\overline{A_0 \oplus B_0})(\overline{A_1 \oplus B_1})$$

Karnaugh-map for  $L$ : Karnaugh map for  $G$ :

	$B_1B_0$	00	01	11	10
$A_1A_0$	00	0	1	0	0
00	00	0	1	0	0
01	00	0	0	0	0
11	00	1	1	0	0
10	00	1	0	0	0

$$L = A_1B_1' + A_1'A_0'B_0 + A_0'B_1'B_0$$

$$= A_1B_1' + A_0'B_0(A_1 + B_1')$$

	$B_1B_0$	00	01	11	10
$A_1A_0$	00	0	0	1	1
00	00	0	0	1	1
01	00	0	1	0	1
11	00	0	0	0	1
10	00	0	0	0	0

$$G = A_1'B_1 + A_0B_1B_0' + A_1'A_0B_0'$$

$$= A_1'B_1 + A_0B_0'(A_1' + B_1)$$

## Circuits

